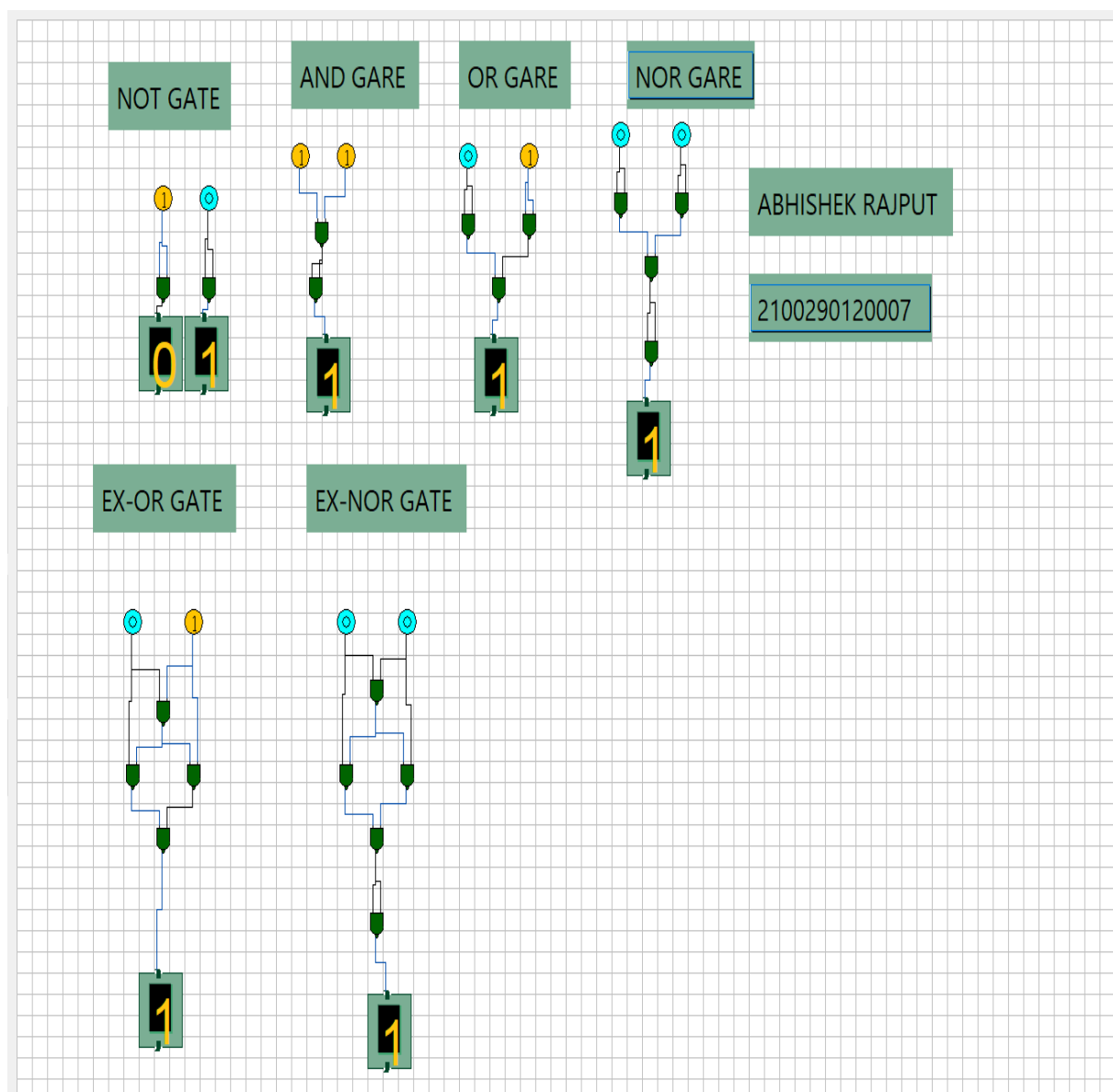# Computer Organization Architecture Lab-KCS-452_2022

ABHISHEK RAJ0UT

2100290120007

IMPLEMENTATION OF LOGIC GATES USING NAND GATE

IMPLEMENTATION OF LOGIC GATES USING NOR GATE

NOT GATE

OR GATE

AND GATE

NAND GATE

ABHISHEK RAJPUT

2100290120007

0

1

0

1

EX-NOR GATE

EX-OR GATE

1

0